
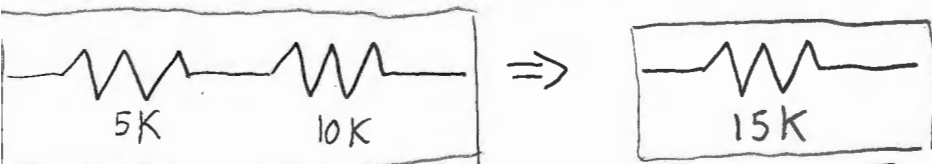


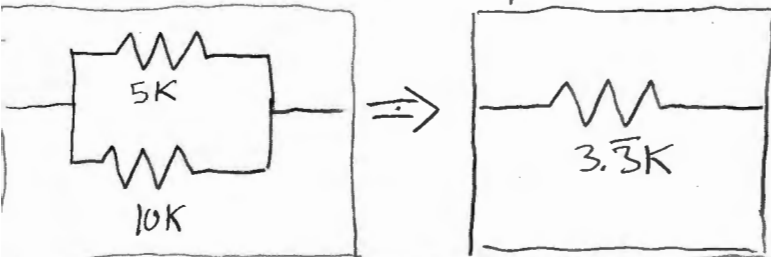1] For resistors in series  $R_{\text{Total}} = \sum_n R_n$



For resistors in parallel  $1/R_{\text{Total}} = \sum_n 1/R_n$

For two resistors in parallel  $R_{\text{Total}} = R_1 R_2 / (R_1 + R_2)$



2]  $R = 1 \Omega$      $V = 12V$      $P = IV = V^2/R = 144W$

3]  $V_{\text{Total}} = \sum_n V_n \Rightarrow IR_{\text{Total}} = \sum_n IR_n = I \sum_n R_n$  (Current is the same through resistors in series)

$$R_{\text{Total}} = \sum_n R_n$$

For resistors in parallel current can vary, but voltage is the same. The current through all of the resistors is the sum of currents through all the resistors.

$$V_{\text{in}} = V_n \quad I_{\text{Total}} = \sum_n I_n \quad V = IR \Rightarrow I = V/R$$

$$\frac{V_{\text{in}}}{R_T} = \sum_n \frac{V_{\text{in}}}{R_n} = V_{\text{in}} \sum_n \frac{1}{R_n}$$


$$\frac{1}{R_T} = \sum_n \frac{1}{R_n}$$

5 | Power rating =  $\frac{1}{4}W = 0.25W$ ,  $R > 1K$   $V = 15V$

$P = \frac{V^2}{R} = \frac{225 \text{ Volts}^2}{R}$  For  $R = 1K = 1000\Omega$   $P = \frac{225}{1000}W = 0.225W$

$0.225W < 0.25W$ , increasing  $R$  only decreases  $P$  for given voltage, and connecting it in various ways can not increase voltage.

10 | Show  $R_{load} = R_{source}$  maximizes power in load for given source resistance  $R_{source} = \text{constant}$

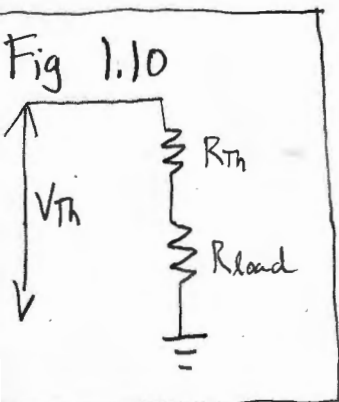

Just before exercise 1.10 under "Power Transfer" it gives  $R_{source} = R_{internal} = R_{Th}$

Want to maximize  $P_L = I_L V_L$

Since  $(R_{Th} = R_s)$  and  $R_L$  are in series  $I_s = I_L = \frac{V_{Th}}{R_s + R_L}$

so  $P_L = \frac{V_{Th}}{R_s + R_L} V_L = \left(\frac{V_{Th}}{R_s + R_L}\right) (I_L R_L) = \left(\frac{V_{Th}}{R_s + R_L}\right)^2 R_L$

$V_{Th}$  is constant and  $R_s = R_{source} = \text{constant}$

To maximize  $P_L$  with respect to  $R_L$ , differentiate with respect to  $R_L$  and set the derivative = 0

$P_L = V_{Th}^2 \frac{R_L}{(R_s + R_L)^2}$

$\frac{\partial P_L}{\partial R_L} = V_{Th}^2 \left[ \frac{(R_s + R_L)^2 - R_L \cdot 2(R_s + R_L)}{(R_s + R_L)^4} \right] = 0$  (Quotient rule)

$(R_s + R_L)^2 - R_L \cdot 2(R_s + R_L) = 0$

$R_s^2 + 2R_s R_L + R_L^2 - 2R_L R_s - 2R_L^2 = 0$

$R_s^2 - R_L^2 = 0$

$R_s^2 = R_L^2$

$R_s = R_L$  (assuming  $R_L \geq 0, R_s \geq 0$ )

To show it is maximum take  $\frac{\partial^2 P_L}{\partial R_L^2}$  and make sure it is less than zero, but that is probably unnecessary.

1.17 Show if  $A = BC$

then

$$|A| = |B||C|$$

where  $A, B, C$  are complex numbers

$$\begin{aligned} A &= a + ib = |A|e^{i\theta} \\ B &= |B|e^{i\phi} \\ C &= |C|e^{i\gamma} \end{aligned}$$

where  $\theta, \phi, \gamma$  are arbitrary

$$A = BC \implies |A|e^{i\theta} = |B|e^{i\phi}|C|e^{i\gamma} = |B||C|e^{i(\phi+\gamma)}$$

since  $A = BC$ ,  $|A|^2 = |BC|^2$

so taking the magnitude of both sides

$$\begin{aligned} \left| |A|e^{i\theta} \right|^2 &= \left| |B||C|e^{i(\phi+\gamma)} \right|^2 \\ &= |A|^2 e^{i(\theta-\theta)} = |B||C|e^{i(\phi+\gamma)} \left( |B||C|e^{-i(\phi+\gamma)} \right) \\ |A|^2 e^{i(\theta-\theta)} &= |B|^2 |C|^2 e^{i(\phi+\gamma-\phi-\gamma)} \end{aligned}$$

$$|A|^2 e^0 = (|B||C|)^2 e^0$$

$$\sqrt{|A|^2} = \sqrt{(|B||C|)^2}$$

$$|A| = |B||C|$$

since magnitudes are real and positive by definition

Q.E.D.